

Reg. No. :

Name :

First Semester M.Sc. Degree Examination, August 2021

Physics

PH 213 : BASIC ELECTRONICS

(2018–19 Admission)

Time : 3 Hours

Max. Marks : 75

PART – A

Answer **any five** questions. Each question carries **3** marks:

- I. (a) How to calculate the power gain of an audio amplifier?
- (b) Which parameters of a BJT limit its high frequency response?
- (c) Explain the difference between first and second order filters.
- (d) Give the design of a 3-bit serial in parallel out shift register.
- (e) Explain the action of a PIN photodiode.
- (f) Explain the working principle and use of a strain gauge.
- (g) Draw the volt-ampere characteristics of a Tunnel Diode and indicate the negative resistance region.
- (h) Explain the working of the LVDT transducer.

(5 × 3 = 15 Marks)

P.T.O.



PART – B

Answer **all** questions, each questions carries **15** marks

- II. A (i) Discuss the frequency response characteristics of a negative feedback amplifier.
- (ii) What are gain and phase margins?

OR

- B (i) Discuss the circuit and working of an operational amplifier based Schmitt Trigger.
- (ii) Show how to design for a particular UTP and LTP **15**

- III. A (i) Discuss the methods of binary arithmetic operations.
- (ii) Give the design of half-adder and full-adder circuits and explain their working.

OR

- B (i) Explain with circuits the operation of asynchronous and synchronous binary counters
- (ii) What are the advantages of synchronous counters? **15**

- IV. A (i) Use suitable block diagrams and explain in detail the working of a Cathode Ray Oscilloscope.
- (ii) How dual trace can be achieved in a CRO?

OR

- B (i) Discuss in detail the structure and working of a semiconductor laser.
- (ii) What is the advantage of using heterojunction in laser diodes? **15**

(3 × 15 = 45 Marks)



PART – C

Answer **any three** questions. Each question carries **5** marks:

- V. (a) An audio amplifier is said to have a voltage gain of 60 dB. If an input signal of 2 mV amplitude is applied then calculate the output voltage.
- (b) An opamp square wave oscillator is required to oscillate at a frequency of 1.5 kHz. Calculate the value of timing resistance if the value of timing capacitor used is $0.22 \mu F$. The feedback factor β is 0.5.
- (c) Give the design of a 3-bit binary ripple counter using J-K flip flops and logic gates which is having a control input for up and down counting modes.
- (d) Give the design of a 10-bit input parity generator circuit.
- (e) A fibre optic cable is 30km long. The measured ratio of input power to output power is 55. Calculate the attenuation of the fibre in dB per km.
- (f) A step index multimode optical fibre is having a core refractive index of 1.55 and cladding refractive index 1.45. Calculate the Numerical Aperture of the fibre.

(3 × 5 = 15 Marks)

